

# Technical Note

**Technical Note Number:** DVC 7-Tech Note-2

**Technical Note Issue Date:** February 18, 2010

**Technical Note Author:** Gary Gotting


**Family:** DVC family

**Models Affected:** DVC 7, DVC 10

**Description:** Connection of PNP or NPN sensors to the digital or Universal inputs


**Background:**

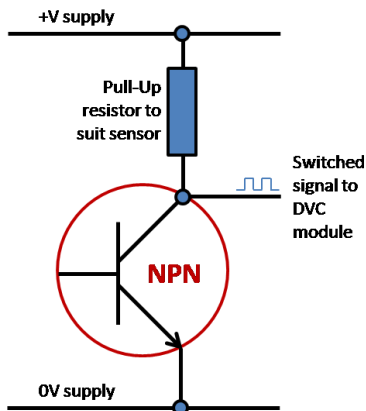- a) Ensuring correct connection and health of DVC inputs and sensor outputs.



**Notes:**

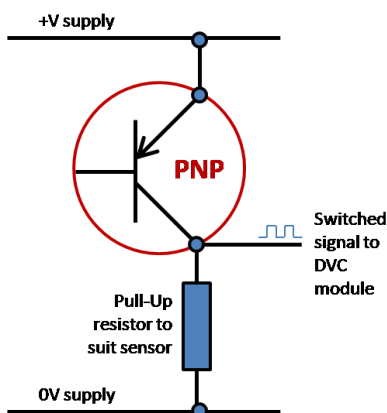1. DVC family universal and analog signal inputs have an internal 1MΩ pull up to +5V resistor fitted ( 5 μA load current ).
2. DVC family have an input impedance of approx 100KΩ on universal and analog signal inputs.
3. If using an NPN style output sensor, EXTERNAL load resistor *may* be required if sensor requires more than 5μA load current.
4. If using a PNP style output sensor, the user MUST use and EXTERNAL load resistor for correct signal.
5. Always refer to sensor manufacturers data sheet for maximum ratings to ensure long sensor life.
6. Some sensors have a minimum switch current requirement to ensure clean output switching. If this is the case, use the minimum current value in the calculation below instead of the 5mA as suggested.



- **Pull up resistor calculation =  $R=V/I$**

Where V is +V supply

Where I is 5mA\*

\*5mA is typical max current value for DVC input requirements